

Assignment 3


Report

Muhammet Fikret ATAR


1801042693

My Logisim design have two circuit files: control.circ and datapath.circ. I combined them in a mult32.circ file to have the 32 bit multiplier.

ASM:

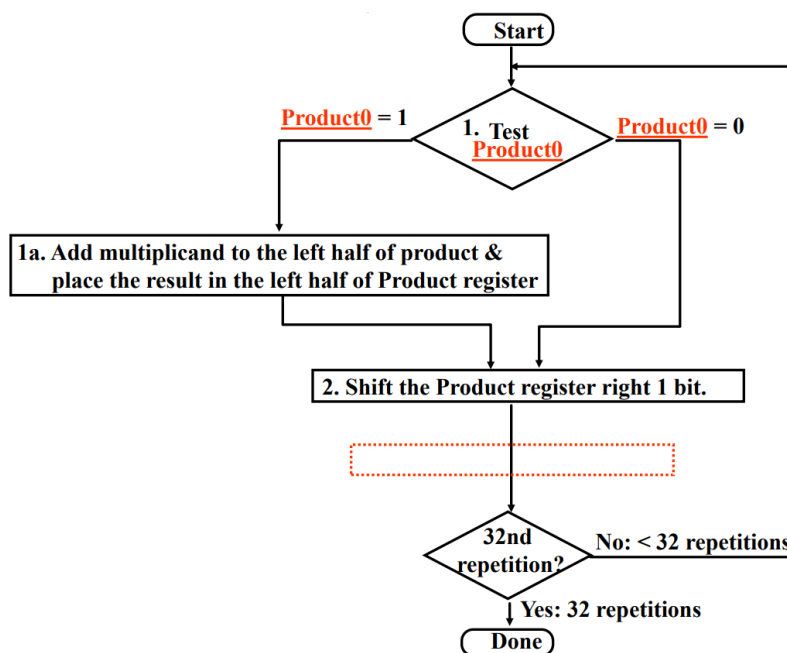

Datapath:

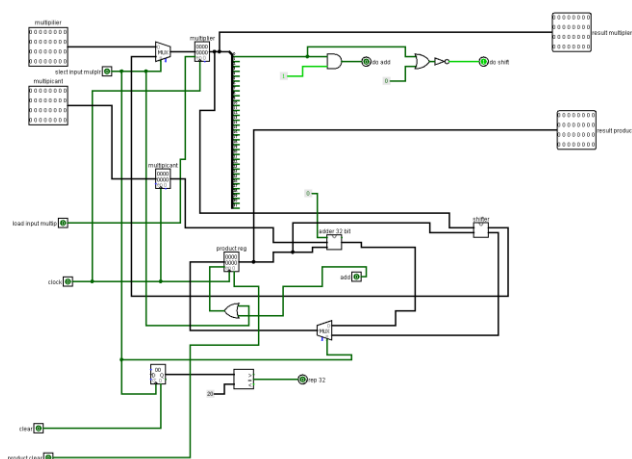

Datapath Input:

- 1-Select input multiplier
- 2.Load Input multiplier
- 3-Clear
- 4-Product Clear
- 5-Add
- 6-Clock

Datapath Output:

1-Do add

2-Do shift

3-Rep 32

Inputs Explanation:

Select input multiplier: This signal determines whether x will get my initial value or the new future value.

Load Input multiplier: This signal determines enable bit of multiplier

Clear: This signal clear counter for restart button

Add : This signal determines product register enable bit with select input multiplier

Outputs Explanation:

Do add : Thanks to the this signal state register jump to add register

Do shift: Thanks to the this signal state register jump to shift register

3-Rep 32 :With this signal, the cycle is terminated.


Control Unit:

Truth Tables inputs/outputs;

P2	P1	P0	Start	Rep32	Restart	D.add	D.Shft	N2	N1	N0
0	0	0	0	-	-	-	-	0	0	0
0	0	0	1	-	-	-	-	0	0	1
0	0	1	-	-	-	1	0	0	1	0
0	0	1	-	-	-	0	1	0	1	1
0	1	0	-	-	-	-	-	0	1	1
0	1	1	-	0	-	-	-	0	0	1
0	1	1	-	1	-	-	-	1	0	0
1	0	0	-	-	0	-	-	1	0	0
1	0	0	-	-	1	-	-	0	0	0

P2	P1	P0	S.I.Multip	Clear	Add	P.Clear	L.I.Multip
0	0	0	0	0	0	1	1
0	0	1	0	0	0	0	0
0	1	0	0	0	1	0	0
0	1	1	1	0	0	0	1
1	0	0	1	1	0	0	0

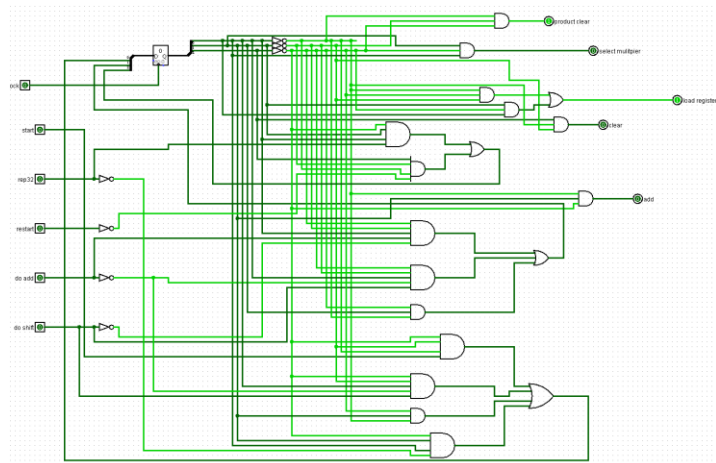I have a control unit consisting of 5 State in total.



Boolean expression:


$N2: P2'P1P0(R32) + P2P1'P0'(Restart)'$

$N1: P2'P1'P0(DOADD)(DOSHIFT)' + P2'P1'P0(DOADD)'(DOSHIFT) + P2'P1P0'$


$N0: P2'P1'P0'(START) + P2'P1'P0(DOADD)'(DOSHIFT) + P2'P1P0' + P2'P1P0(R32)'$

Tests:


2089*1

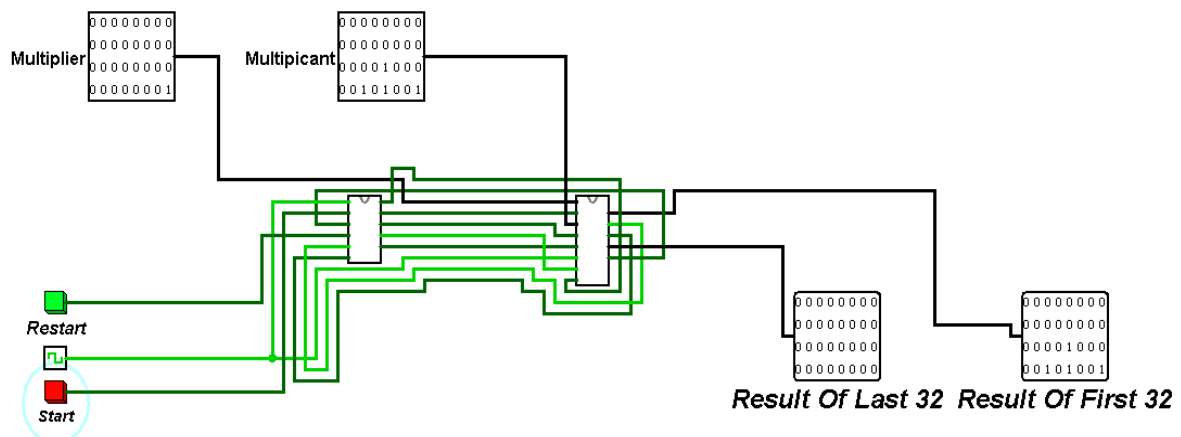


$$2^{31} * 2^{31} = 2^{62}$$

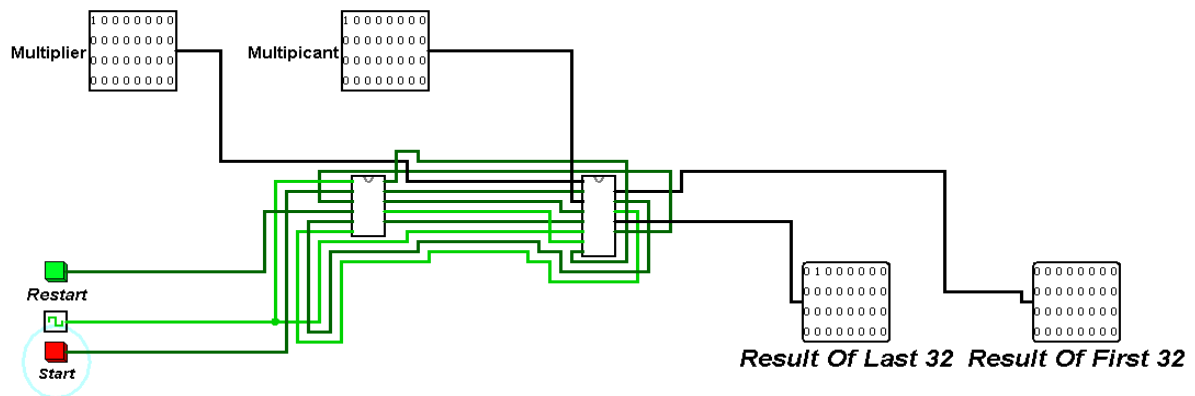


$$1044 * 4628 = 4831632$$

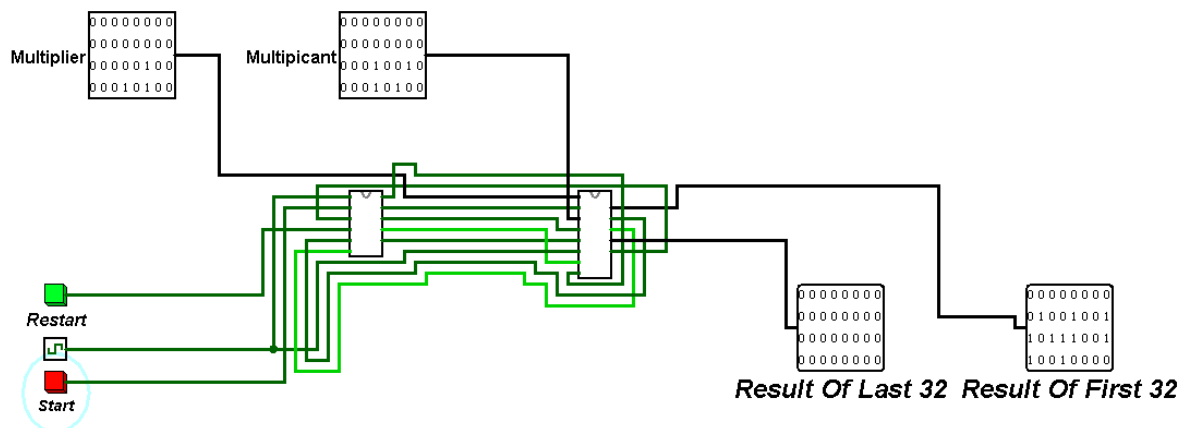


$$15 * 15 = 225$$

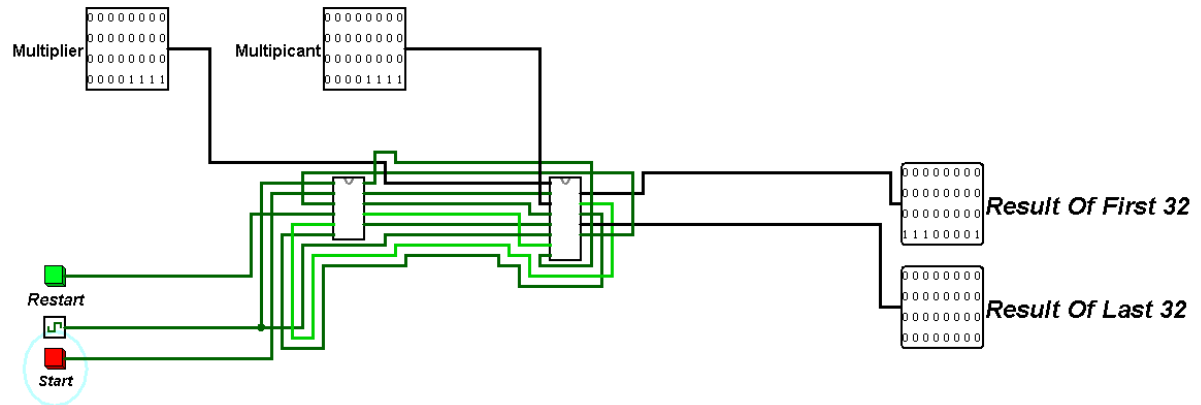

$$5 * 8 = 40$$

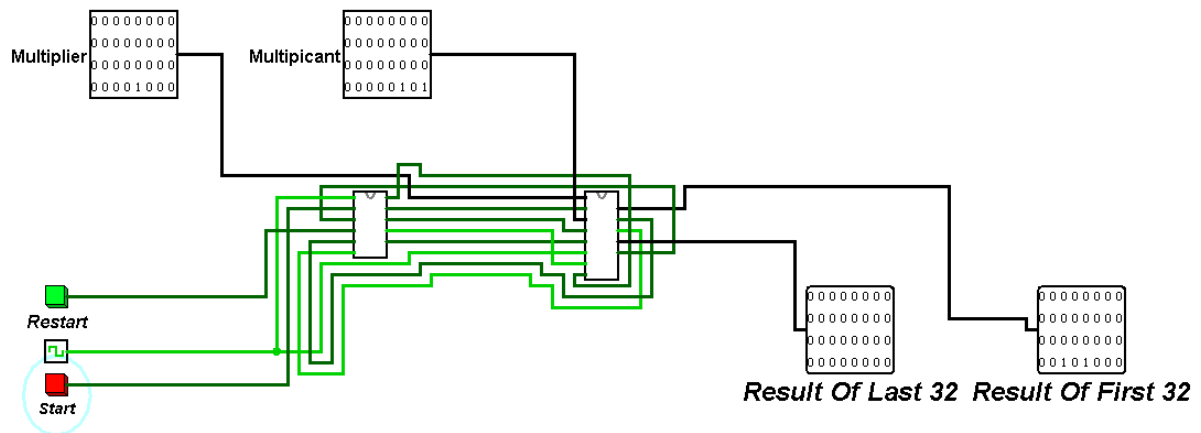


$$3 \times 3 = 9$$

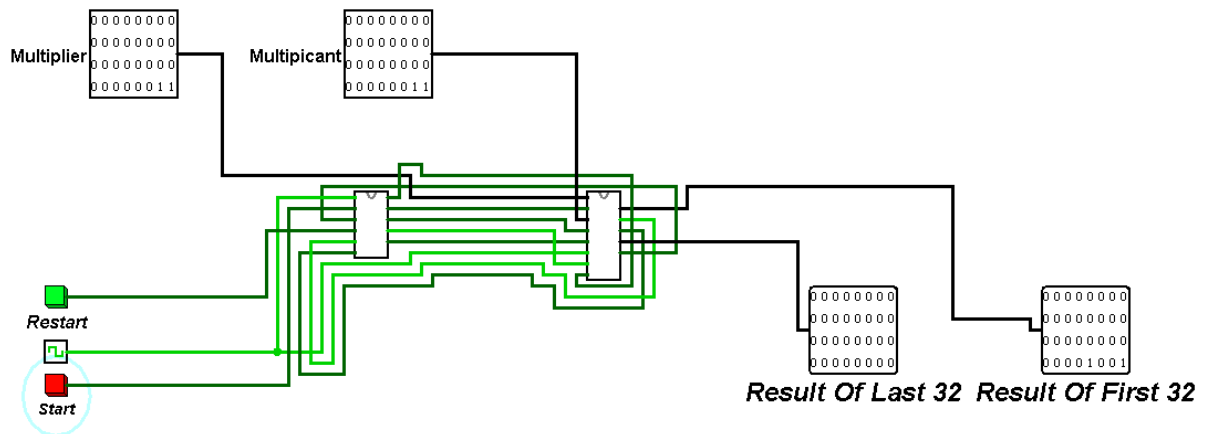


Bonus Part:

Shifter:

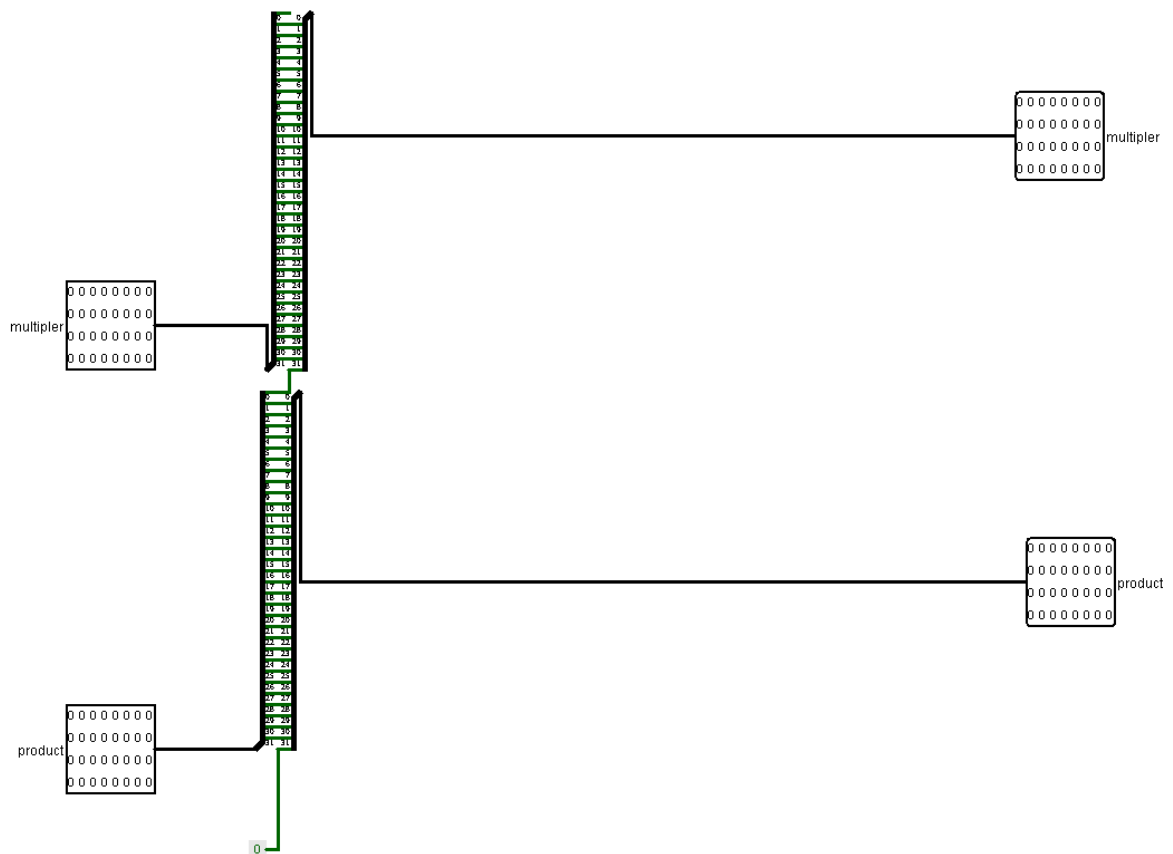

1 Bit Adder:

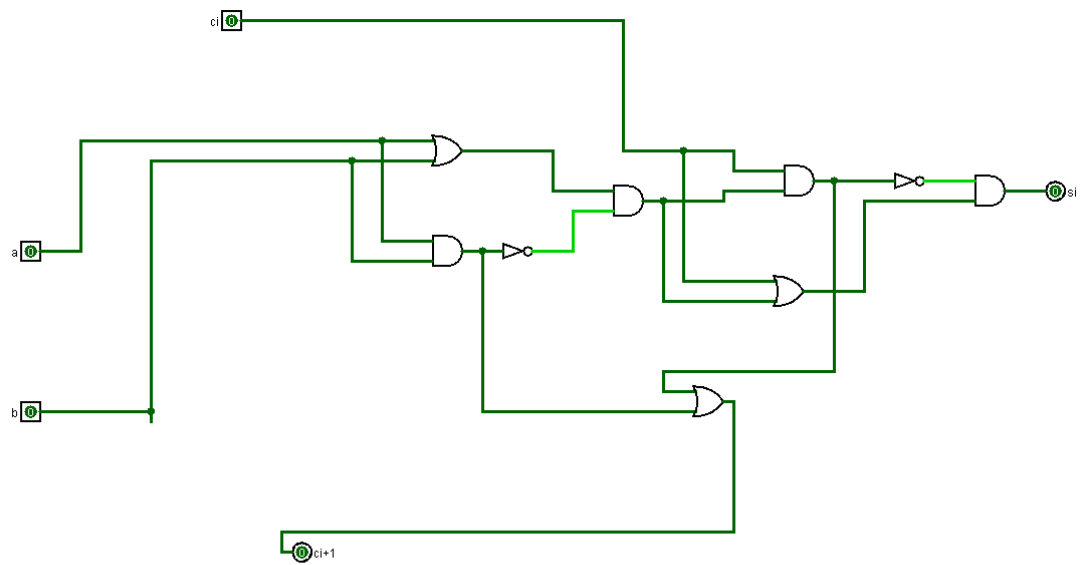

32 Bit Adder:

